

MIPS 1 in VHDL

HDL Lab - SS 2015

Bahri Enis Demirtel, Carlos Minamisava Faria, Lukas Jäger, Patrick Appenheimer



TECHNISCHE
UNIVERSITÄT
DARMSTADT

Fachbereich Elektrotechnik und Infor-
mationstechnik
Fachgebiet Integrated Electronic
Systems Lab

Contents

1	Introduction	1
1.1	Task	1
2	Design	2
2.1	ALU	2
2.2	Datapath	3
2.2.1	Instruction fetch	3
2.2.2	Instruction decode	3
2.2.3	Execution	5
2.2.4	Memory Stage	5
2.2.5	Writeback	5
2.3	Controlpath	5
3	Evaluation	6
4	Synthesis	7
5	Conclusion	8

1 Introduction

In the HDL Lab is a practical exercise of a hdl language implementation. This semester the task is the implementation of a MIPS I microcontroller in vhdl. A requirement to this laboratory is the lecture HDL: Verilog and VHDL from Prof. Dr.-Ing. Klaus Hofmann.

The MIPS instruction set is a reduced instruction set computer (RISC). There are available references for 32 and 64-bit with many revisions. This microcontroller reference is often used as an hdl first project.

1.1 Task

The objective is to design, implement, synthesise and test a MIPS-I specified processor core on FPGA. The hardware description language is VHDL and the target technology is a Virtex5 from Xilinx. The synthesised microcontroller must be able to run at 50 MHz with a desirable frequency of 200 MHz. The microcontroller must use a pipeline of a minimum of 2 and maximum of 6 stages. The following subcomponents are mandatory: ALU, datapath and controlpath.

2 Design

This chapter describes the design of a MIPS 1 microcontroller. A microcontroller consists mostly of a processor core, memory and programmable inputs/outputs peripherals. This design implementation focus only on the processor core design.

This laboratory requires a microcontroller structure of at least a CPU containing a controlpath, datapath and an ALU. The created design uses this base with a 5-staged pipeline. The CPU interacts with two external memories and has also a clock and a reset input. All of which are considered external to this design. The CPU is divided in two base components: a control and a datapath block, as shown in Figure 2.1.

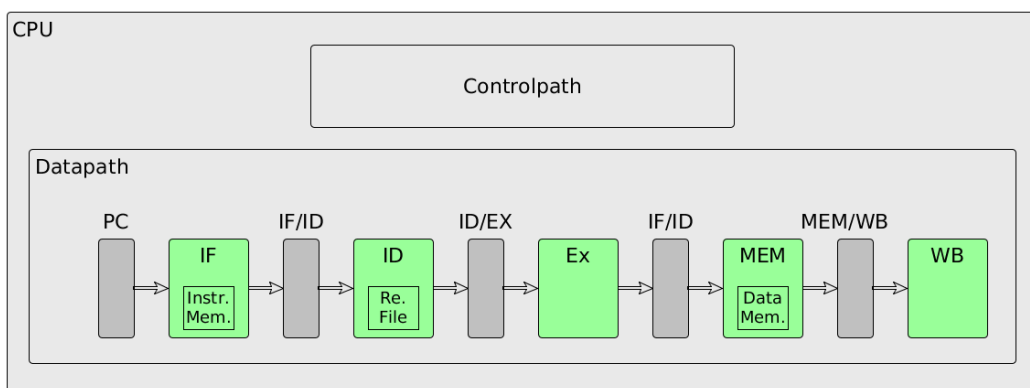


Figure 2.1: Datapath pipeline

In the datapath there is the pipeline made of five blocks: instruction fetch (IF), instruction decode (ID), execution (EX), memory stage (Me) and writeback (WB).

The following sections describe the central component ALU and the two base components: datapath and controlpath. The cpu components structure is shown in Figure 2.2:

 


Figure 2.2: CPU component structure

2.1 ALU

2.2 Datapath

This section describes the datapath and its internal elements. The datapath is the component that connects the pipeline components within itself as well as with cpu inputs and outputs and the controlpath.

This MIPS implementation works with a 5 stage pipeline in order to achieve a fast clock. The datapath consists of instruction fetch, instruction decode, execution, memory stage and writeback. The datapath controls the information flow from one pipeline stage to the next with registers. These writing process occur on the positive edge of the clock when the pipeline stage input from the controlpath. That is, the registers forwards information synchronously. The datapath forwards the controlpath signals asynchronously, contrary to the pipeline to pipeline signals.

 


Figure 2.3: Datapath pipeline

The program counter (PC) is programmed into the datapath. Its function is to store the current program address, which is mostly counted up. It has a multiplexer controlled by the controlpath to choose the input. The two possible inputs are to count up (PC+4) from instruction fetch and the jump or branch from instruction decode. The controlpath chooses always the instruction decode input in the case of jump or branch.

The following subsections describe the pipeline components as well as its functions and IOs.

2.2.1 Instruction fetch

This first block of the pipeline is the instruction fetch. The main task of this block is to fetch the next instruction and pass it further to the pipeline.

The program counter is a 32-bit input, which is directly outputted as instruction address to fetch an instruction. The instruction fetch inputs the program memory's instruction data, with the actual 32-bit instruction. This value is directly forwarded to the pipeline.

The program counter is also incremented by four, because the used memory is 8-bit long. This incremented value is given back to PC.

2.2.2 Instruction decode

The second block of the pipeline is the instruction decode. Its main tasks are to divide the instruction into its pieces, manage the register file and manage branches.

The main input is the instruction from the instruction fetch stage. This instruction is 32-bit long and can be of three types. These are shown in Table 2.1 [1].

The **opcode** indicates the operation or arithmetic family of operations. Opcode equals zero are the R-type operations. The field **funct** provides a specific operation. **rs**, **rt** and **rd** provide sources or destinations register addresses. **shamt** indicates the shift amount for shift operations. **immediate** carries a relative address or constant, which is zero or sign extended to 32-bits. **address** is an absolute address.

The main outputs are register A, register B, shift, immediate and IP. Other than IP, all outputs depend on the instruction decoding.

Table 2.1: MIPS instruction types

Type	format (bits)					
R	opcode (6)	rs (5)	rt (5)	rd (5)	shat (5)	funct (6)
I	opcode (6)	rs (5)	rt (5)	immediate (16)		
J	opcode (6)	address (26)				

Register File

The register file is a set of 32 general purpose 32-bit registers. These have the advantage, comparing to the ram memory, that they can always be accessed within one clock cycle. The access to these registers is made with five bits, which allows multiple registers to be referenced per instruction. All loaded memory values are stored in a register for later use.

The registers are numbered from \$0 through \$31. There is also a convention for using these registers, which must be enforced by assembly language and follow Table 2.2 [2]:

Table 2.2: MIPS registers

Register Number	Conventional Name	Usage
\$0	\$zero	Hard-wired to 0
\$1	\$at	Reserved for pseudo-instructions
\$2 - \$3	\$v0, \$v1	Return values from functions
\$4 - \$7	\$a0 - \$a3	Arguments fo functions - not preserved by subprograms
\$8 - \$15	\$t0 - \$t7	Temporary data, not preserved by subprograms
\$16 - \$23	\$s0 - \$s7	Saved registers, preserved by subprograms
\$24 - \$25	\$t8 - \$t9	More temporary registers, nor preserved by subprograms
\$26 - \$27	\$k0 - \$k1	Reserved for kernel. Dot not use.
\$28	\$gp	Global Area Pointer (base of global data segment)
\$29	\$gp	Stack pointer
\$30	\$sp	Frame Pointer
\$31	\$ra	Return Address

This implementation of MIPS does not have a FPU. In case of FPUs another 32 32-bit register set is used.

The register file is written on the clock's negative edge with writeback information. The register file require a 5-bit destination register address and the 32-bit word to be written into the register.

Branch Logic

The branch and jump instructions require just one clock between instruction fetch and the jump itself. Due to this constrain, there is the need of a branch logic inside the instruction decode part. The output of this operation is the next instruction address for PC.

On the jump command, PC will receive the jump value. In case of a branch, PC will receive either the branch value or PC+4, depending on the instruction decode decision. This behaviour allows for the controlpath always to activate the instruction decode input in cases of jumps and branches.

Forwarding

Often calculated or memory read values are used in the following instructions. Due to the pipeline, the values are not ready in the register file, causing a data hazard. In order to avoid this conflict a data forwarding system is integrated. The data forwarding provide separated inputs for the 5-bit destination register address and the 32-bit word for the ALU, memory stage and writeback.

2.2.3 Execution

This stage of the pipeline takes care of the actual mathematical operations. It provides two main multiplexers, one for each value input of the ALU. The inputs of the first multiplexer are the zero padded shift input, the number four (32-bit) and the register A from instructino decode. The second multiplexer provides register B, the immediate value and IP as inputs.

Both multiplexers are controlled by the controlpath.

2.2.4 Memory Stage

The memory stage is the fourth block of the pipeline and has the main task of fetch or save in the memory.

For memory operations the execution stage outputs two 32-bit values: `aluResult_in`, which works as the memory address, and `data_in`, which is data to be written in the memory. On read operations, the `data_to_cpu` input delivers the 32-bit memory value.

This stage has one multiplexer choosing the pipeline stage output from `aluResult_in` or `data_to_cpu`.

2.2.5 Writeback

This writeback stage is the fifth and last stage of the pipeline. Its main task is just to hold the calculated values, as well as the values read from the memory so they can be written the register file.

2.3 Controlpath

3 Evaluation

The cpu evaluation is done with Modelsim from MentorGraphics. Individual testbenches were created to test each separate cpu component as well as for the complete cpu.

The complete cpu passed the complete simulation with a simulated perfect memory, that means without either instruction or data access stalls. Furthermore it also passed the simulation with a simulated real memory.

For the implementation on the fpga a hdlab code was prepared with the cpu, memory, uart and pll components already integrated as well as the LEDs, clock and reset interface with the fpga. The cpu passed this simulation with the counter program, outputting the counter value to the LEDs output.

4 Synthesis

5 Conclusion

Bibliography

- [1] MIPS Technologies Inc. *MIPS32™ Architecture For Programmers Volume I: Introduction to the MIPS32™ Architecture*. 2001.
- [2] Jason W. Bacon. Computer science 315 lecture notes, 2011.